
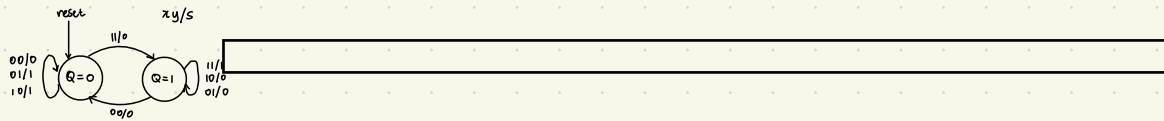


Problem 1

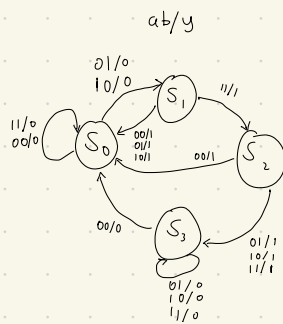


Problem 3




Problem 4

circuit1 w/ <=

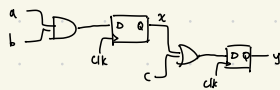

circuit1 w/ =

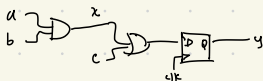

circuit2 w/ <=



circuit2 w/ =

