

CSE 371 Lab 4 Report


Elijah Melton, 2164822

Ankith Tunuguntla, 2234509

Design Procedure ASMD


bit_counter ASMD

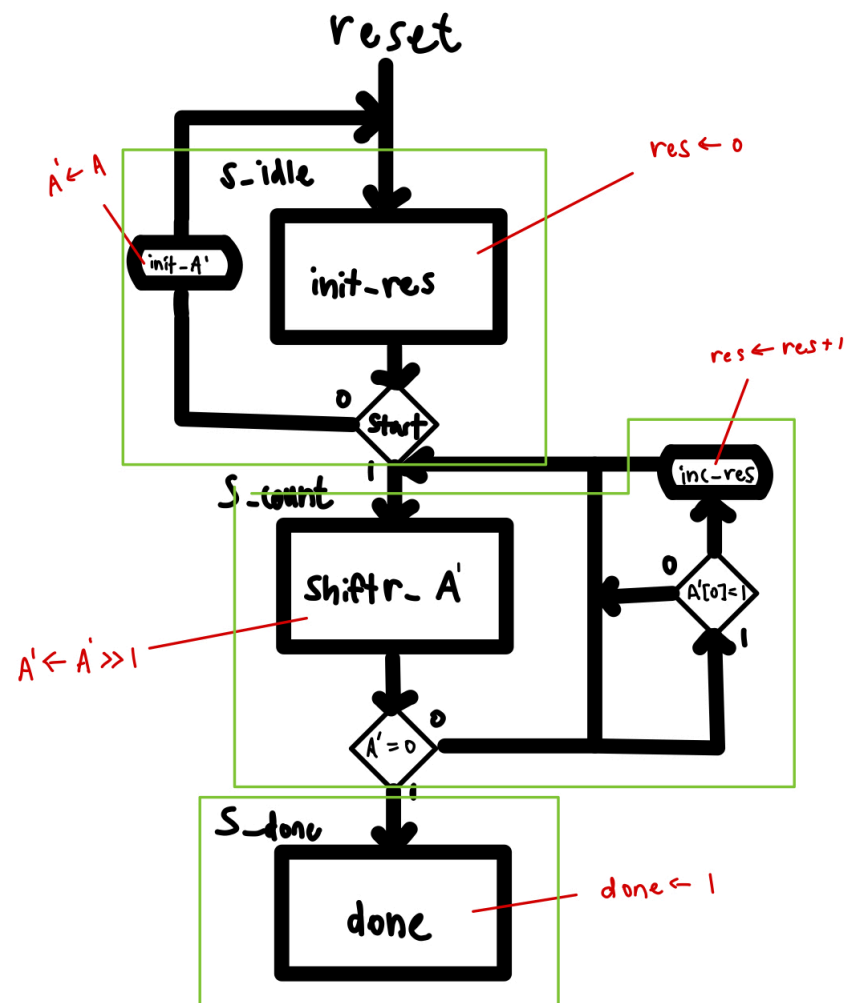Our ASMD for bit counting. Green is the ASM blocks, RTL is written in red.




part1 Block Diagram

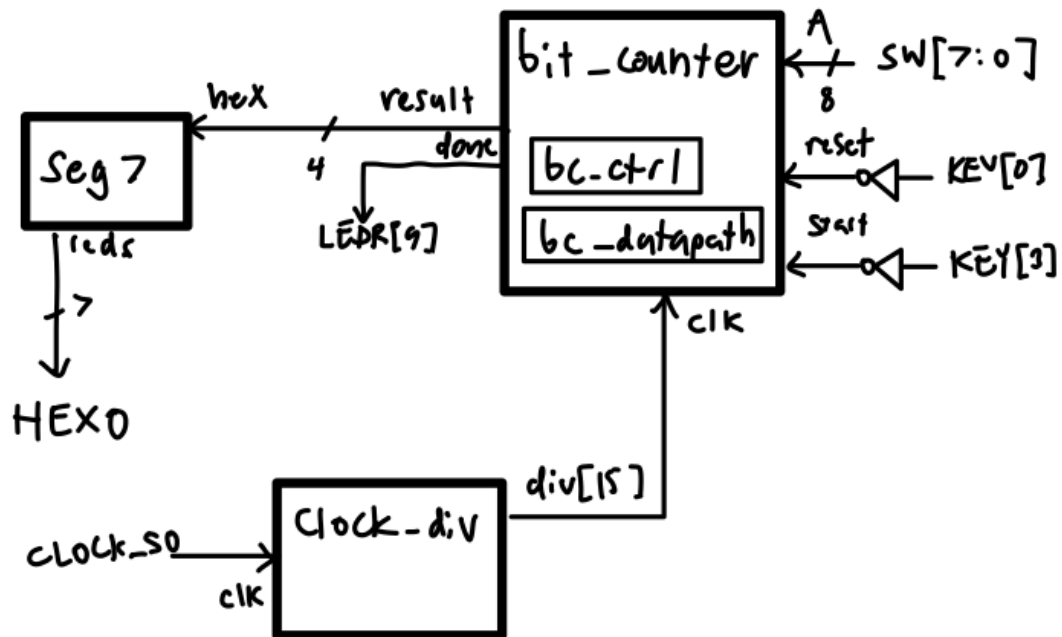Block diagram for just bit counting top level module with SW 0-7 for input, KEY 0 for reset, KEY 3 for start, and HEX 0 for the result. Also includes LEDR 9 to show done




binary_search ASMD

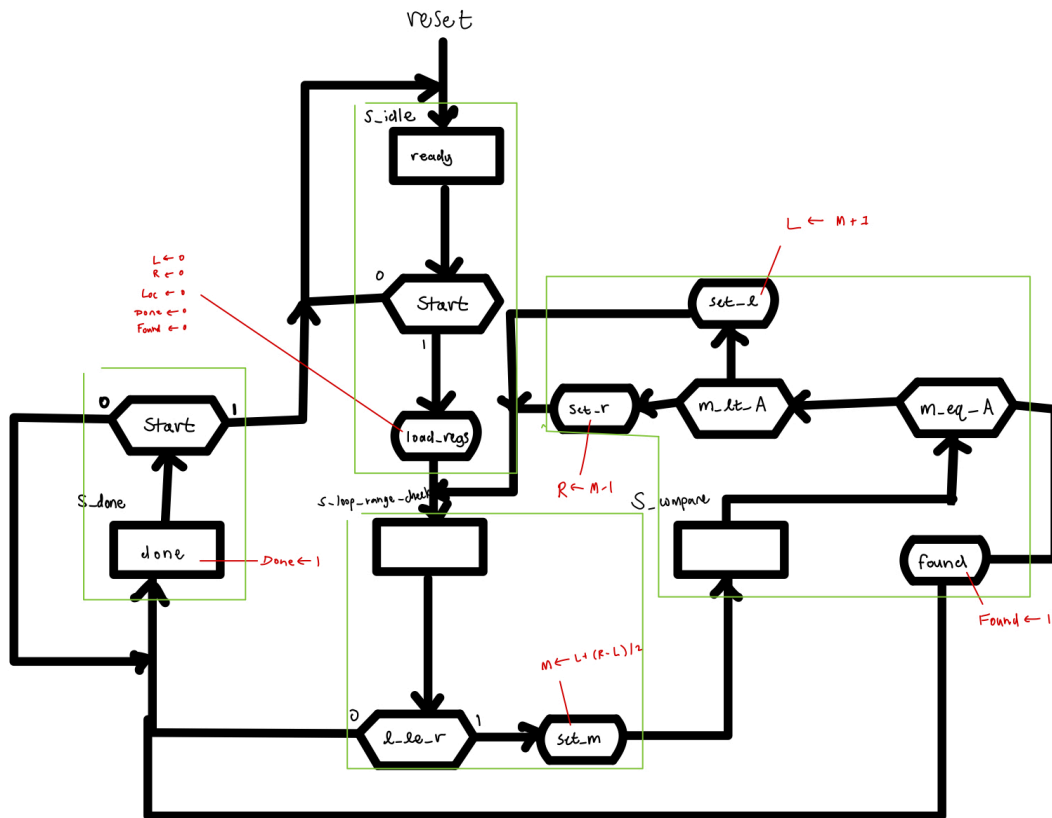Our ASMD for binary search. Green is the ASM blocks, RTL is written in red.




part2 Block Diagram

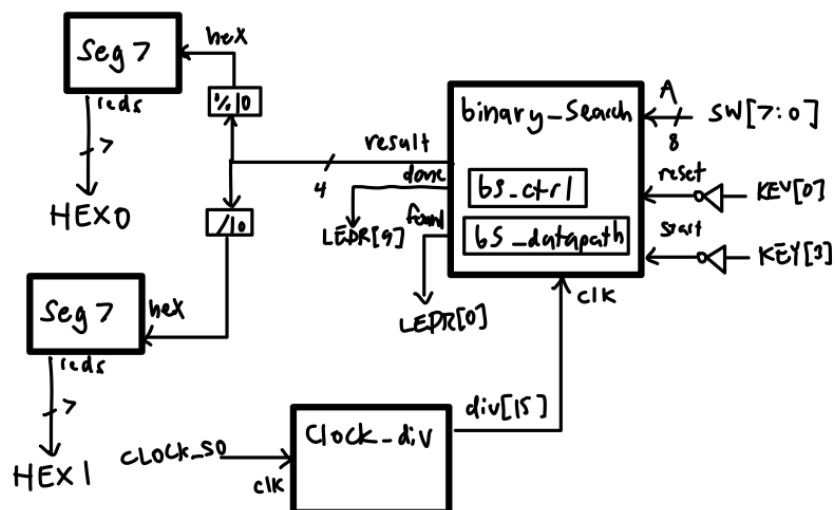Block diagram for just binary search top level with SW 0-7 for input, KEY 0 for reset KEY 3 for start, and HEX 0-1 for showing the result. Also includes LEDR 9 to show done and LEDR 0 for showing found



both Block Diagram

Diagram for combined binary search and bit counting, muxed with SW[9] with all other inputs and outputs the same

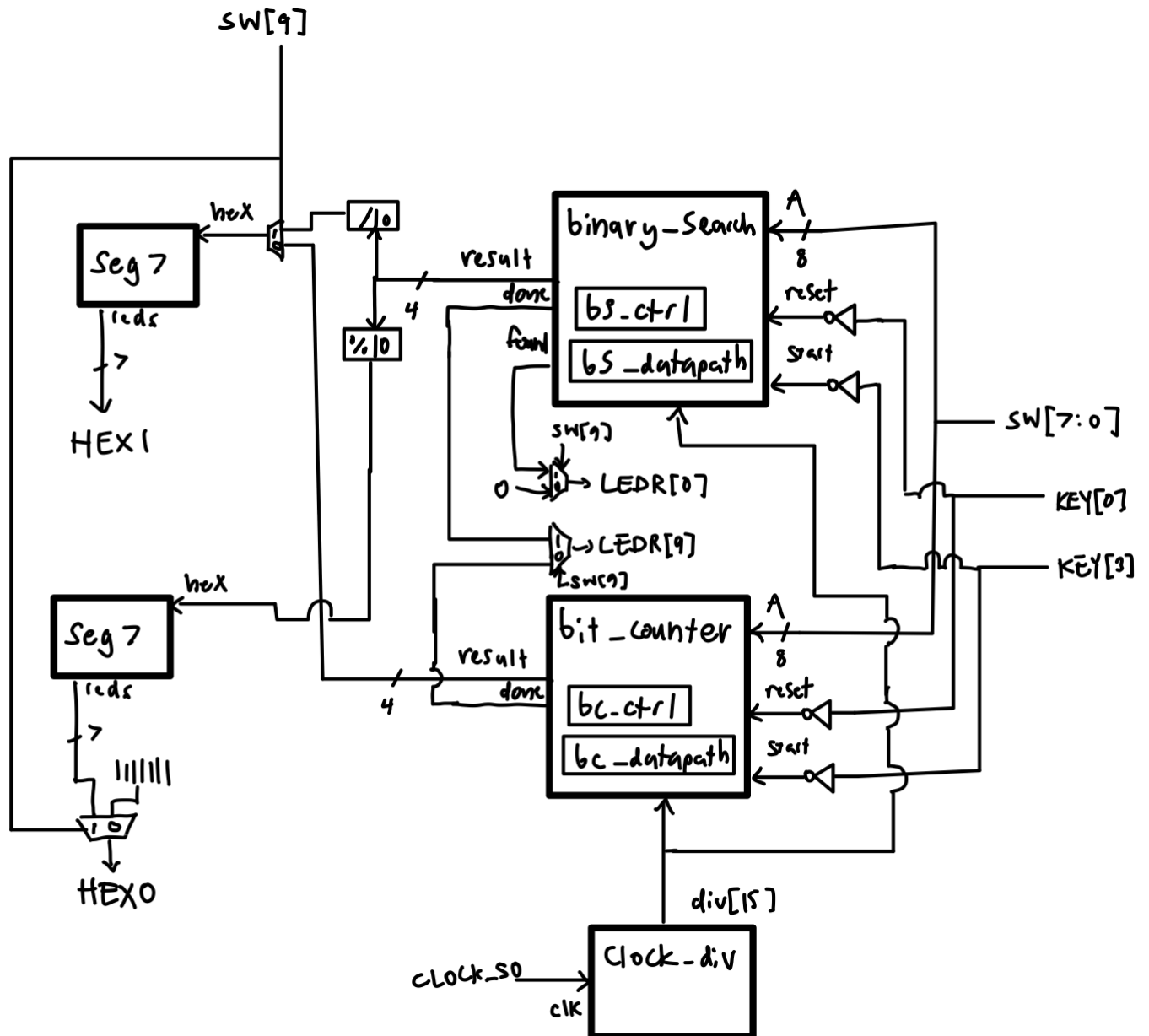

Results

Our implementation ended up being pretty similar to our design, with mostly only minor differences (signal names), as well as a few notable changes for handling reset (perform init datapath logic on reset). We used a clock divider, and also made sure to use a start loop to handle metastability.

We separated both algorithms into 3 modules as we did in lecture: `*_ctrl`, `*_datapath`, and `*`, where `*` is the algorithm. Then, in our top level modules we simply instantiated the `*` module, along with a `clock_div` and `seg7` and all the required hardware mappings.

To multiplex between the two algorithms, we used a single `always_comb` block with default initializations, and then two cases for `SW[9]` that toggle between outputs of the given algorithm.


bit_counter_tb simulation

With the input `10101010`, it correctly outputs 4.

With the input `01010101`, it correctly outputs 4.


With the input `11111111`, it correctly outputs 8.

 With the input `00000000`, it correctly outputs 0.




binary_search simulation

 - First I search for 15, and find it in one loop.
- Then I search for 31 and find it in 5



- Then I search for 0 and find it in 5

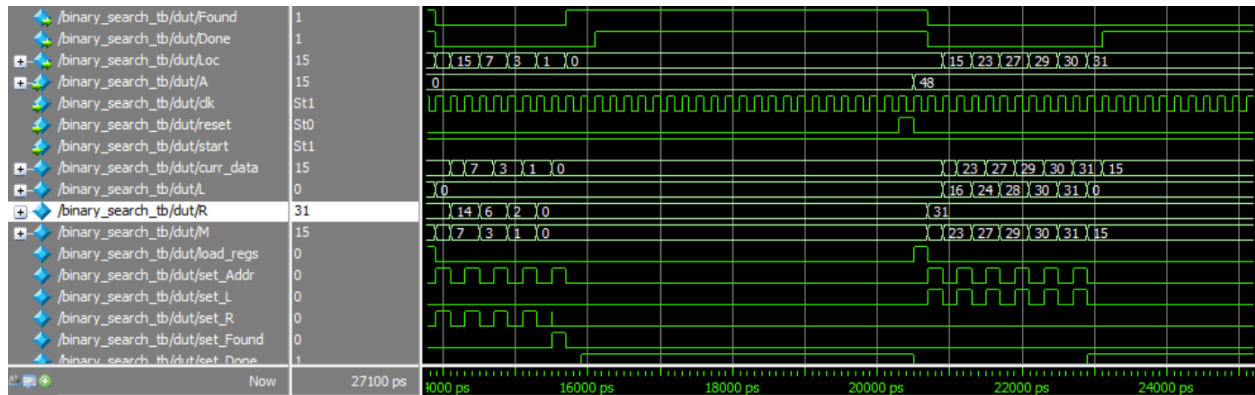- Finally, I search for 48, which doesn't exist and tests an overflow edge case. It correctly ends with Done but not Found asserted



Experience Report

Feedback

This lab was fairly easy compared to the previous ones, but still challenging since I am fairly new to implementing ASMD

Significant Issues

None to speak of

Tips/Tricks

- Write pseudo code and the signals out before making a diagram
- Test all edge cases of the algorithms
- Avoid overflow when finding midpoint with $a + (b - a) / 2$ trick

Time Spent

~11 hours